

MARCH 2006, APPLIED ELECTRONICS, PAPER 1

Ques 1 (A): Select correct alternative and rewrite the following sub question – (4 Marks)

- a) In SMPS _____ feedback is used.
- (i) Positive (ii) Negative (iii) Positive and negative (iv) None
- b) If supply voltage to IC555 AMV is reduced to half, then its output frequency _____.
- (i) Is double the original frequency (ii) Is half the original frequency (iii) Does not change (iv) Is two third the original frequency
- c) If a Lissajou's pattern like 8 is obtained, then frequency to vertical input f_y and frequency to horizontal input f_x are related by the equation _____.
- (i) $f_y = 2f_x$ (ii) $f_x = 2f_y$ (iii) $f_x = f_y$ (iv) None of the above
- d) The secondaries in L VDT have equal number of turns, but they are connected in _____.
- (i) Parallel (ii) Series assisting (iii) Series opposition (iv) None of the above

Ques 1 (B): Attempt any TWO of the following – (6 Marks)

- a) In an OPAMP differentiator, feedback resistor is equal to 2 M and input capacitor is 3 F. Find output voltage is input voltage changes from 0.1 V to 0.6 V within 5 seconds.
- b) Define amplitude modulation Give the expression for modulated output and draw waveform.
- c) Draw the pin configuration and symbol of IC 741.

Ques 2 (A): Attempt any TWO of the following – (6 Marks)

- a) With neat circuit diagram, explain the working of sweep generator.
- b) The turns ratio of a transformer used in a bridge rectifier is $n_1:n_2 = 10:1$. The primary is connected to the AC mains. Assuming ideal diodes, calculate the output voltage, and PIV rating of the diodes.
- c) Explain the concept of virtual ground in OPAMP.

Ques 2 (B): Attempt any ONE of the following – (4 Marks)

- a) Draw the block diagram of cellular radio and explain function of each block in brief.
- b) Explain the working of inverting OPAMP with neat circuit diagram and derive expression for its gain.

Ques 3 (A): Attempt any TWO of the following – (6 Marks)

- a) Draw and explain the I-V graph of zener diode.
- b) State various frequency ranges in an electromagnetic spectrum.
- c) Draw a circuit diagram of monostable multivibrator using IC 555 and explain its working.

Ques 3 (B): Attempt any ONE of the following – (4 Marks)

- a) Define common mode rejection ratio and slew rate for an OPAMP. Explain their effect on the performance of an OPAMP.
- b) Explain with a neat figure, how CRO displays a waveform.

Ques 4 (A): Attempt any TWO of the following – (6 Marks)

- a) Explain Low CRO is used to measure AC and DC voltages.
- b) Explain three factors to be considered for selection of transducer.
- c) Draw the pin configuration of LM 317 and state the expression for its output voltage.

Ques 4 (B): Attempt any ONE of the following – (4 Marks)

- Explain the four characteristics of a regulated power supply.
- Draw a neat block diagram of a fibre-optic communication system and explain its working.

Ques 5 (A): Attempt any TWO of the following – (6 Marks)

- Explain the working of an opto coupler with neat diagram.
- In an inverting adder, calculate output voltage if input voltage is 500mV input resistor is $1k\Omega$ and feedback resistance is ten times the input resistance.
- List various communication networks and explain one.

Ques 5 (B): Attempt any ONE of the following – (4 Marks)

- Explain the working of function generator with neat block diagram.
- Explain the working of a centre-tapped full wave rectifier with neat diagram and waveforms.

OR

Ques 5 (A): Attempt any TWO of the following – (6 Marks)

- Define active and passive transducers and give one example of each.
- With the help of a neat circuit diagram, explain the working of a voltage follower using OPAMP.
- Explain the use of satellite as a relay station with neat diagram.

Ques 5 (B): Attempt any ONE of the following – (4 Marks)

- With neat circuit diagram, derive the output expression for an OP AMP subtractor.
 - Explain with diagram and waveforms, working of LC filter for eliminating ripple.
-