

## MARCH 2008, DIGITAL ELECTRONICS, PAPER 2

**Ques 1 (A): Select correct alternative and rewrite the following sub question – (4 Marks)**

- a) The equivalent decimal number of a maximum highest binary number of length one byte is \_\_\_\_\_
- (i) 128                      (ii) 127                      (iii) 255                      (iv) 256
- b) An AND gate in positive logic becomes \_\_\_\_\_ gate in negative logic.
- (i) OR                      (ii) NOR                      (iii) NOT                      (iv) NAND
- c) Shift Register belongs to the class of \_\_\_\_\_
- (i) Combinational logic circuit      (ii) Sequential logic circuit      (iii) Both i) and ii)      (iv) None of the above
- d) In a \_\_\_\_\_ type ADC, more than one comparators are used.
- (i) Successive Approximation      (ii) Simultaneous      (iii) Counter      (iv) None of the above

**Ques 1 (B): Attempt any TWO of the following – (6 Marks)**

- a) Subtract the following numbers by using 2's complement method :
- i)  $(11011)_2 - (011)_2$       ii)  $(10111)_2 - (110001)_2$
- b) Convert the following :
- i)  $(11011)_2 = (?)_{10}$       ii)  $(F6.C9)_{16} = (?)_2$       iii)  $(110\ 110\ 110.\ 110)_2 = (?)_{16}$

**Ques 2 (A): Attempt any TWO of the following – (6 Marks)**

- a) What are Universal Building Blocks ? How the basic gates are constructed using NOR gates only?
- b) Simplify the following:  $Y = ABC + ABC + ABC$ , Draw the logic diagram for simplified expression.
- c) Explain the working of clocked SR flip-flop using NAND gates.

**Ques 2 (B): Attempt any ONE of the following – (4 Marks)**

- a) Define radix or base of a number system. Explain with suitable example Hex-dabble method used for converting decimal number to hexadecimal number.
- b) What are the various codes used in digital system?  
What is their necessity? How many possible combinations are there in each code?

**Ques 3 (A): Attempt any TWO of the following – (6 Marks)**

- a) Explain the following parameters of digital ICs:
- i) Propagation delay      ii) Fan out      iii) Figure of merit.
- b) Explain the working of CMOS NOR gate with diagram.
- c) Explain the working 1:4 demultiplexer using logic gates.

**Ques 3 (B): Attempt any ONE of the following – (4 Marks)**

- a) State and prove De Morgan's Theorems.
- b) Define full adder. Draw a logic diagram of full adder. Write its Boolean equations and truth table

**Ques 4 (A): Attempt any TWO of the following – (6 Marks)**

- What is a Multiplexer? Design a 4:1 multiplexer using 2:1 multiplexers.
- What is a Decoder? Explain BCD to Decimal decoder using appropriate logic gate.
- Explain the need of Multiplexing and Demultiplexing.

**Ques 4 (B): Attempt any ONE of the following – (4 Marks)**

- Draw a well labeled diagram of digital computer. Explain the function of each block.
- Name various input and output devices used in computer.

**Ques 5 (A): Attempt any TWO of the following – (6 Marks)**

- Explain J-K flip-flop with the help of logic diagram.
- Draw circuit diagram of weighted resistor type DAC. Explain its working.
- Explain working of T flip-flop with suitable diagram.

**Ques 5 (B): Attempt any ONE of the following – (4 Marks)**

- Explain the working of TTL NAND with open collector output.
- What will be the output voltage of a 4 bit R-2R ladder, corresponding to the binary. Given: Logic 0 corresponds to 0 volts and logic 1 corresponds to 8 volts.

**OR**

**Ques 5 (A): Attempt any TWO of the following – (6 Marks)**

- Explain the working of counter type ADC.
- Explain the working of right shift register using D flip-flops.
- Explain the working of Decimal of BCD encoder using OR gates.

**Ques 5 (B): Attempt any ONE of the following – (4 Marks)**

- Draw a neat block diagram of asynchronous decade counter. Explain its working.
- Implement the following multi-output combinational logic circuit using a 4 : 16 line decoder circuit.

$$F_1 = m(1,2,4,7,8,11,12,13)$$

$$F_2 = m(2,3,9,11)$$

$$F_3 = m(10,12,13,14)$$