

MARCH 2010, APPLIED ELECTRONICS, PAPER 1

Ques 1 (A): Select correct alternative and rewrite the following sub question – (4 Marks)

- a) In SMPS the transistor is used as _____.
- (i) An amplifier (ii) An oscillator (iii) **A switch** (iv) A rectifier
- b) Pulse width of a MMV with $R = 10k\Omega$ and $C = 0.22\mu F$ will be _____.
- (i) **2.42ms** (ii) 2.42 μs (iii) 2.42sec (iv) 24.2ms
- c) In an electromagnetic spectrum, visible light ranges from _____.
- (i) 4–7 μm (ii) **0.4–0.7 μm** (iii) 0.4–0.7mm (iv) 0.4–0.7nm
- d) Piezoelectric transducer is _____ transducer.
- (i) Temperature (ii) **Pressure** (iii) Photo (iv) Chemical

Ques 1 (B): Attempt any TWO of the following – (6 Marks)

- a) Explain with neat circuit diagram the function of time base generator used in CRO.
- b) What are the types of deflection systems used in CRT? Explain principle of any one.
- c) State and explain function of any three front panel controls used in CRO.

Ques 2 (A): Attempt any TWO of the following – (6 Marks)

- a) Explain the following terms with reference to CRO: fluorescence, phosphorescence, aquadag coating.
- b) Draw and explain functional block diagram of three terminal IC voltage regulator.
- c) In half wave rectifier circuit, primary is connected to 230V AC. The turns ratio of transformer used is 10:1. Calculate output DC voltage, output DC current for a load of 2k Ω .

Ques 2 (B): Attempt any ONE of the following – (4 Marks)

- a) Draw block diagram of opamp and explain working of each block.
- b) Explain Schmitt trigger with neat circuit diagram. Draw transfer curve and define hysteresis.

Ques 3 (A): Attempt any TWO of the following – (6 Marks)

- a) Draw a neat labeled diagram of CRT and explain.
- b) In a zener regulator find series resistance, zener current, load current if $V_{in} = 30V$, $V_z = 20V$, total current in the circuit is 30mA.
- c) With a neat circuit diagram explain opamp as subtractor and derive expression for the output voltage.

Ques 3 (B): Attempt any ONE of the following – (4 Marks)

- a) Explain working of FSK generator using IC 555.
- b) In an AMV if $R_1 = 5k\Omega$, $R_2 = 3k\Omega$, $C = 0.2\mu F$, calculate on time, off time, percentage duty cycle and frequency of the circuit.

Ques 4 (A): Attempt any TWO of the following – (6 Marks)

- a) Explain working of inverting amplifier using opamp and derive expression for output voltage.
- b) Find output voltage in an inverting adder if $V_1 = 0.2V$, $V_2 = 0.5V$, $V_3 = 0.4V$, $R_1 = 1k\Omega$, $R_2 = 2k\Omega$, $R_3 = 5k\Omega$ and $R_f = 10k\Omega$.
- c) With the help of neat labeled diagram explain construction and working of loudspeaker.

Ques 4 (B): Attempt any ONE of the following – (4 Marks)

- a) Explain series regulator with current limiting.
- b) Draw and explain neat circuit diagram of a bridge rectifier. Also draw input output waveforms.

Ques 5 (A): Attempt any TWO of the following – (6 Marks)

- a) What is modulation? Explain need of modulation.
- b) What is geostationary satellite? Explain use of satellite as relay station.
- c) Explain serial and parallel data communication systems.

Ques 5 (B): Attempt any ONE of the following – (4 Marks)

- a) Explain opamp integrator and differentiator circuit. Also state expression for output voltage.
- b) Draw a neat diagram of function generator and explain function of each block.

OR

Ques 5 (A): Attempt any TWO of the following – (6 Marks)

- a) Explain three factors to be considered while selecting a transducer for a particular application.
- b) Compare amplitude modulation with frequency modulation.
- c) Explain the following opamp parameters with suitable diagram: input offset current, input bias current, CMRR.

Ques 5 (B): Attempt any ONE of the following – (4 Marks)

- a) List any four advantages of fiber optic cable over conventional electrical cables.
- b) Explain simplex and duplex communication systems with suitable example of each.
