

OCTOBER 2008, APPLIED ELECTRONICS, PAPER 1

Ques 1 (A): Select correct alternative and rewrite the following sub question – (4 Marks)

- a) In CRT _____ anode has variable positive voltage.
- (i) Pre-accelerating (ii) Focusing (iii) Accelerating (iv) Control Grid
- b) For bridge rectifier current rating of diode is equal to _____
- (i) I_{dc} (ii) I_{dc} (iii) I_{dc} (iv) None of the above
- c) The output impedance of an ideal OP-AMP is _____
- (i) Infinite (ii) Zero (iii) 57Ω (iv) 75Ω
- d) _____ network configuration has fastest speed.
- (i) Star (ii) Bus (iii) Ring (iv) All

Ques 1 (B): Attempt any TWO of the following – (6 Marks)

- a) List the types of filters used in power supply. Explain the working of anyone type in detail.
- b) In OP-AMP inverting amplifier feedback resistor of $10k\Omega$ is used. Find the input resistance to get 10 times input at output. Draw its circuit diagram.
- c) Define Amplitude, Frequency and Phase Modulation.

Ques 2 (A): Attempt any TWO of the following – (6 Marks)

- a) Explain the working of Time-base Generator using UJT. Draw the Waveform and state the equation of its frequency.
- b) Explain with the help of circuit diagram, how Zener Diode is used as voltage regulator?
- c) Draw the symbol of Operational Amplifier and show the pin connections of IC 741.

Ques 2 (B): Attempt any ONE of the following – (4 Marks)

- a) What is the principle of LVDT? Explain its construction and write it's working.
- b) Explain in details how OP-AMP is used as Schmitt Trigger. Draw circuit diagram and its transfer characteristic.

Ques 3 (A): Attempt any TWO of the following – (6 Marks)

- a) Enlist the application of CRO. Explain anyone in detail.
- b) In a centre tapped full wave rectifier secondary voltage is $6V$ AC. Using ideal diodes, calculate the dc load voltage, load current, if load resistance of 54Ω is connected.
- c) State any six ideal characteristics of OP-AMP.

Ques 3 (B): Attempt any ONE of the following – (4 Marks)

- a) Define for FM.
- i) Frequency Deviation ii) Modulation Index
iii) Deviation Ratio iv) Percentage Modulation
- b) Draw the block diagram of Operational Amplifier and explain its working.

Ques 4 (A): Attempt any TWO of the following – (6 Marks)

- a) Explain the factors considered for selection of a Transducer.
- b) Draw the labeled circuit diagrams of OP-AMP as Integrator and Differentiator, State their output equations.
- c) In AM, carrier voltage increases to $150V$ and reduces to $30V$ due to modulating signal. Calculate Modulation Index.

Ques 4 (B): Attempt any ONE of the following – (4 Marks)

- Draw the functional block diagram of DMM and explain its working.
- Write basis idea of Switched Mode Power Supply (SMPS). State its advantages. (any four)

Ques 5 (A): Attempt any TWO of the following – (6 Marks)

- Explain working of optocoupler using diagram.
- Explain the working of monostable multivibrator using IC555. Draw its circuit diagram.
- In an inverting adder, if $R_1 = 2k\Omega$, $R_2 = 10k\Omega$ and $R_3 = 5k\Omega$ with $V_1 = 2V$, $V_2 = -4V$ and $V_3 = 5V$, then calculate the output voltage if $R_f = 10k\Omega$.

Ques 5 (B): Attempt any ONE of the following – (4 Marks)

- Explain the working of transistorized series regulator using its circuit diagram.
- Draw the block diagram of fiber optic communication System. Explain its working.

OR

Ques 5 (A): Attempt any TWO of the following – (6 Marks)

- Explain the working of FSK using IC 555. Draw its circuit diagram.
- Define for opamp: slew rate, CMRR, input bias current.
- State and explain any three characteristics of Power Supply.

Ques 5 (B): Attempt any ONE of the following – (4 Marks)

- Draw block diagram of Function Generator and describe function of each block in brief.
- With the help of block diagram, explain cellular radio system.