

## OCTOBER 2008, DIGITAL ELECTRONICS, PAPER 2

**Ques 1 (A): Select correct alternative and rewrite the following sub question – (4 Marks)**

- a) The equivalent decimal number of a maximum binary number of length on byte is \_\_\_\_\_.
- (i) 8                                      (ii) 64                                      (iii) 255                                      (iv) 256
- b) The gate ideally suited for bit comparison is \_\_\_\_\_.
- (i) Two input exclusive NOR Gate      (ii) Two input exclusive OR Gate      (iii) Two input NAND Gate      (iv) Two input NOR Gate.
- c) \_\_\_\_\_ Flip-flop is used to avoid race around condition.
- (i) RS                                      (ii) JK                                      (iii) JK MS                                      (iv) None of the above
- d) A/D Converter which does not use DAC is \_\_\_\_\_.
- (i) Simultaneous ADC      (ii) Counter type ADC      (iii) Successive Approx. type ADC      (iv) None of the above

**Ques 1 (B): Attempt any TWO of the following – (6 Marks)**

- a) Convert :
- i)  $(117.6 C)_{16} = ( \quad )_2$   
ii)  $(13.3125)_{10} = ( \quad )_{16} = ( \quad )_2$
- b) Show that using Boolean Algebra and De-Morgan's theorem.
- i)  $BC + DAC + DABC + DBC = C$   
ii)  $A(A+C)(AB+C) = 0$
- c) Explain the concept of clock in digital circuit; hence explain the working of D-FF.

**Ques 2 (A): Attempt any TWO of the following – (6 Marks)**

- a) State and prove De-Morgan's Theorem.  
b) What are Derived Gates? Draw symbols and write the truth table of each.  
c) Explain the working of Ring Counter.

**Ques 2 (B): Attempt any ONE of the following – (4 Marks)**

- a) Write a note on EBCDIC Code.  
b) Subtract the following numbers using 2s complement subtraction 4  
i)  $1011 - 101$     ii)  $11.01 - 10.111$     iii)  $11011 - 1100$     iv)  $10111.1 - 10011.1$

**Ques 3 (A): Attempt any TWO of the following – (6 Marks)**

- a) Define the following :
- i) Propagation Delay    ii) Noise Margin    iii) Figure of merit for digital IC
- b) Explain the working of CMOS NAND Gate.  
c) What is a Multiplexer? Explain how a 4:1 Mux can be simulated using simple 4 way single pole switches.

**Ques 3 (B): Attempt any ONE of the following – (4 Marks)**

- a) Add binary numbers 1001 and 0100 using 4 bit binary adder. Explain its working.  
b) What is an Ex-OR Gate? Give its symbol, truth table and explain how it is used as a parity checker.

**Ques 4 (A): Attempt any TWO of the following – (6 Marks)**

- The  $D_0$  and  $D_3$  inputs of a 4:1 Mux are connected to logic-0 and  $D_1$  and  $D_2$  inputs are connected to logic-1. Explain in brief what type of logic function the Mux will perform? When select input are given values 0 and 1 in different, combinations.
- Explain the working of Seven Segment Decoder Driver.
- What is an Encoder? Explain the working of decimal to BCD encoder using OR Gates.

**Ques 4 (B): Attempt any ONE of the following – (4 Marks)**

- Write notes on Floppy Disc, CD ROM.
- Draw basic block diagram of Computer and state the function of each block.

**Ques 5 (A): Attempt any TWO of the following – (6 Marks)**

- Explain the working of Right Shift Register.
- In 4 bit R-2R ladder DAC find Full Scale Output Voltage and Analog Output Voltage for 1010 input.
- A clock signal of 128 kHz is applied at the input of a binary counter. Frequency at the output of last flip-flop is 2kHz. What will be the maximum number of counts that can be recorded by this counter?

**Ques 5 (B): Attempt any ONE of the following – (4 Marks)**

- Explain the working of TTL NOR Gate. What is the significance of diode in it?
- Explain the working of Simultaneous ADC.

**OR**

**Ques 5 (A): Attempt any TWO of the following – (6 Marks)**

- Explain the working of Binary Weighted Resistor type DAC.
- Explain the working of Edge Triggered T- Flip-flop.
- What is Decoder? Explain BCD to Decimal Decoder.

**Ques 5 (B): Attempt any ONE of the following – (4 Marks)**

- Explain the working of 4 bit Binary Ripple Counter.
- Implement the following multi-output combinational logic circuit using 4 to 16 line decoder.  
 $F_1 = m(1,2,4,7,8,11,12,13)$   
 $F_2 = m(2,3,9,11)$   
 $F_3 = m(10,12,13,14)$