

OCTOBER 2009, APPLIED ELECTRONICS, PAPER 1

Ques 1 (A): Select correct alternative and rewrite the following sub question – (4 Marks)

- a) Electro statically deflect CRT is used in _____.
- (i) Computer monitor (ii) TV picture tube (iii) **CRO** (iv) RADAR
- b) Working principle of light dependent resistor is based on _____.
- (i) Photo emissive effect (ii) **Photo conductive effect** (iii) Photo voltaic effect (iv) None of the these
- c) In frequency response curve, at cutoff frequency gain is _____ % of maximum gain.
- (i) 0 (ii) 50 (iii) **70.7** (iv) None of these
- d) For perfect amplitude modulation index M is equal to _____.
- (i) **One** (ii) Greater than one (iii) Less than one (iv) Zero

Ques 1 (B): Attempt any TWO of the following – (6 Marks)

- a) Draw basic block diagram of regulated power supply and explain function of each block.
- b) Define the following terms for opamp: input bias current, CMRR.
- c) With circuit diagram and relation for output frequency explain a stable multivibrator using IC555.

Ques 2 (A): Attempt any TWO of the following – (6 Marks)

- a) The spot on CRT is shifted by 4cm when 10V DC is applied to its vertical input. Find maximum displacement of spot when 10V AC is applied.
- b) List transducers used to measure temperature and explain active temperature transducer.
- c) State and explain necessity of modulation (any three points).

Ques 2 (B): Attempt any ONE of the following – (4 Marks)

- a) With circuit diagram explain use of zener diode as voltage regulator.
- b) Explain opamp as zero reference and reference voltage comparator with the help of circuit diagrams.

Ques 3 (A): Attempt any TWO of the following – (6 Marks)

- a) With diagram explain how CRO displays waveforms.
- b) Draw block diagram of 3-terminal voltage regulator IC and explain function of each block.
- c) With the help of circuit diagram and derivation explain opamp as inverting amplifier.

Ques 3 (B): Attempt any ONE of the following – (4 Marks)

- a) Explain the following opamp applications: integrator, differentiator.
- b) List different types of network topologies and explain two network topologies.

Ques 4 (A): Attempt any TWO of the following – (6 Marks)

- a) Explain working of photo relay circuit using LDR.
- b) With the help of diagram explain opamp as voltage follower.
- c) A carrier wave of frequency 1810kHz and peak value of 60V is amplitude modulated by 2kHz audio wave of amplitude 30V. Determine modulation index and bandwidth of modulated signal.

Ques 4 (B): Attempt any ONE of the following – (4 Marks)

- a) Draw block diagram of DMM and explain its working.
- b) In a half wave rectifier using transformer, secondary voltage is 12V and load resistance is 100Ω. Then calculate DC voltage, DC current, peak AC voltage and PIV of the diode.

Ques 5 (A): Attempt any TWO of the following –

(6 Marks)

- Compare any three parameters in case of center tapped transformer full wave rectifier circuit and bridge rectifier circuit.
- Explain concept of virtual ground in opamp.
- Explain with circuit diagram the working of frequency shift keying generator using IC 555.

Ques 5 (B): Attempt any ONE of the following –

(4 Marks)

- Explain with diagram the use of CRO in measurement of: phase difference between two signals, unknown frequency.
- What is amplitude modulation? State expression for modulated wave and draw waveform of modulated wave.

OR

Ques 5 (A): Attempt any TWO of the following –

(6 Marks)

- Explain I-V characteristics of zener diode with the help of circuit diagram.
- What are the active and passive transducers? Give example of each.
- In opamp inverting adder if $R_1 = 1\text{k}\Omega$, $R_2 = 2\text{k}\Omega$, $R_3 = 3\text{k}\Omega$ and $R_f = 6\text{k}\Omega$, calculate output voltage for $V_1 = V_2 = V_3 = 0.3\text{V}$.

Ques 5 (B): Attempt any ONE of the following –

(4 Marks)

- Explain working of cellular radio phone with simple block diagram.
- In an AMV if $R_2 = 750\Omega$ which is connected between pin-7 and pin-6 & pin-2, determine the value of resistor R_1 connected between pin-7 and positive line. Also determine the value of timing capacitor C, if output frequency is 1MHz and duty cycle of the circuit is 80%.