

Ques 1: A) Fill in the blanks by choosing the *correct* alternative –

(4)

- a) If one diode in BR is open, the circuit still works as _____. FWR, BR, Filter Circuit, HWR
- b) When _____ of IC 555 is grounded, it stops its working. pin-7, pin-1, pin-8, pin-4
- c) _____ transducer is known as dual type of transducer. thermister, LVDT, Piezo crystal, gas sensor
- d) The transmitter-receiver combination in satellite is known as _____. walkie-talkie, GPS, SMT, transponder

B) Attempt any TWO of the following:

(6)

- a) Define: input bias current, input offset voltage and frequency response for opamp.
- b) Draw the block diagram of DMM and explain the function of various blocks, in brief.
- c) Explain how CRO can be used to measure the phase using Lissajou's patterns.

Ques 2: A) Attempt any TWO of the following –

(6)

- a) Explain the working of FWR with circuit and waveforms.
- b) What is fiber-optic communication? Explain with diagram.
- c) Explain using circuit diagram, the working of comparator using IC741 as opamp.

B) Attempt any ONE of the following –

(4)

- a) Explain the working of LVDT with neat diagram.
- b) Explain the working of capacitor filter circuit with circuit diagram.

Ques 3: A) Attempt any TWO of the following -

(6)

- a) How the opamp can be used as integrator? Derive output equation with circuit diagram and waveforms.
- b) Draw the block diagram of a simple Function Generator and explain its working.
- c) Explain with the help of *suitable diagram* principle working of cellular radio system.

B) Attempt any ONE of the following –

(4)

- a) Draw the block diagram of CRO, and explain the function of each block.
- b) What is thermister? Explain its working with Wheatstone bridge circuit.

Ques 4 A) Attempt any TWO of the following –

(6)

- a) Draw circuit diagram of two transistors regulator circuit and explain its working.
- b) Explain loudspeaker as a transducer, with diagram.
- c) Draw circuit diagram of subtractor and derive its output expression.

B) Attempt any ONE of the following –

(4)

- a) How satellite can be used as relay station? Explain the working of transponder with diagram.
- b) Draw the block diagram of fax machine and explain its working in brief.

Ques 5 A) Attempt any TWO of the following –

(6)

- a) State *any six* merits of FM over AM.
- b) Compare magnetic and electrostatic deflection systems used in CRO with diagrams and give its equation.
- c) Explain working of LAN with any one example and diagram.

B) Attempt any ONE of the following –

(4)

- a) Draw the internal block diagram of opamp and explain the function of each block.
- b) Explain in brief the basic concept of Pulsed RADAR.

OR

Ques 5 A) Attempt any TWO of the following –

(6)

- a) Draw opamp as adder and find V_o if $V_1 = 20\text{mV}$, $V_2 = 45\text{mV}$ and $V_3 = 500\mu\text{V}$, consider that $R_1 = R_2$.
- b) Calculate the output frequency of IC555 as AMV, if $R_1=1\text{k}\Omega$, $R_2= 470\text{k}\Omega$ and $C = 1.2\text{nF}$.
- c) Explain any three characteristics of a DC power supply.

B) Attempt any ONE of the following –

(4)

- a) Design voltage regulator using IC LM 340 for $V_o =12\text{V}$, (if $V_{\text{ref}}= 1.25\text{V}$) and $R_1 = 2\text{k}\Omega$.
- b) Draw block diagram of 3-terminal voltage regulator IC LM317 and explain its working.

Guessing Paper (2017 Exam)

Subject: Digital Electronics – II, XII Electronics

Time: 3 Hrs

Marks: 50

Ques 1: A) Select correct alternative and rewrite the sentence: (4)

- a) The binary value of $(111100110111.101100000001)_2$ will be _____.
(F37.B01)₁₆, (F37.110)₁₆, (E47.C01)₁₆, (101.B01)₁₆
- b) When any one input of Ex-OR gate is at logic-1, the circuit acts as _____.
NOR gate, NAND gate, NOT gate, Ex-OR gate
- c) The number of flip-flops required for MOD-117 counter will be _____.
Nine, five, seven, sixty-four
- d) Total number of resistors required in a n-bit weighted resistor network is given by _____.
 2^n , $1-2^n$, 2^{n-1} , 2^n-1

B) Attempt any TWO of the following – (6)

- a) Explain the working of counter type A/D converter circuit using diagram. Consider 4-bit output.
- b) What is decoder? Explain decimal to BCD decoder using IC 7446/7447 with diagram.
- c) Why NOR gate is called UBB? Explain how it can be used to construct basic gates.

Ques 2: A) Attempt any TWO of the following – (6)

- a) Explain hex-dabble method with any one example.
- b) What is the memory in computer? State the different types of memory devices used in computer.
- c) Convert the given numbers into binary: $(23.8)_{10}$, $(95.30)_{10}$, $(124.1)_{10}$

B) Attempt any ONE of the following – (4)

- a) In a circuit of 4-bit R-2R ladder find: (a) full scale output (b) for input 1101, if 0 = 0V and 1 = 16V.
- b) Design 8:1 multiplexer using two 4:1 multiplexer circuits and explain its working with diagram table.

Ques 3: A) Attempt any TWO of the following – (6)

- a) Mention various types of volatile memories.
- b) Draw the circuit of CMOS NOR gate and explain its working.
- c) How controlled inverter circuit works using Ex-OR gates? Draw its circuit and explain the working.

B) Attempt any ONE of the following – (4)

- a) What is a demultiplexer? Design 1:4 Demux using gates and explain its working.
- b) State and prove De Morgan's both theorems.

Ques 4: A) Attempt any TWO of the following – (6)

- a) Draw the circuit of M/S flip-flop and explain its working.
- b) Draw the circuit of 16:1 line mux with detailed labels.
- c) What is a shift register? Explain any one type of register, with circuit diagram.

B) Attempt any ONE of the following – (4)

- a) Draw the circuit of 3-bit, asynchronous counter and explain its working with wave diagrams.
- b) Draw the diagram of encoder using IC 7447 and explain its working.

Ques 5: A) Attempt any TWO of the following – (6)

- a) Mention the classification of logic families.
- b) What is Mux? Draw the circuit of 4:1 Mux using switch and explain it. Draw its logic diagram also.
- c) Draw the circuit of controlled inverter and explain its working. How it is useful in adder/subtractor circuit?

B) Attempt any ONE of the following – (4)

- a) Define: power dissipation, figure of merit, fan out, propagation delay.
- b) Discuss the working of 4-bit binary adder using circuit diagram.

OR

Ques 5: A) Attempt any TWO of the following – (6)

- a) Explain the process of successive approximation method, with circuit and the necessary steps.
- b) Using 2's complement method, explain the process of subtraction of any two binary numbers with an example.
- c) Draw the block diagram of computer and explain it in brief.

B) Attempt any ONE of the following - (4)

- a) Compare TTL and CMOS logic circuits with any four points.
- b) Prove the following identities: (1) $(\bar{A} + B + C)(A + \bar{B} + C)(A + B + \bar{C}) = AB + BC + AC + \bar{A}\bar{B}\bar{C}$
(2) $(\bar{A} + B)(\bar{B} + C)(A + \bar{C}) = ABC + \bar{A}\bar{B}\bar{C}$