

- Ques 1 A]** Fill in the blanks by choosing the *correct* alternative – [4]
- a) In FWR, current in each diode flows for _____ of the input signal.
half cycle, full cycle, quarter cycle, none of these
- b) The _____ pin of the timer IC 555, is known as reset pin.
pin-7, pin-1, pin-8, pin-4
- c) Capacitive transducer is a _____ transducer.
Heat, light, displacement, gas
- d) In _____ communication system, bidirectional communication is possible.
duplex system, baseband system, simplex system, triplex system
- B]** Attempt any **TWO** of the following: [6]
- a) Explain how CRO can be used to measure the frequency using Lissajou's patterns.
- b) Draw the block diagram of function generator and explain the various block functions in brief.
- c) Define: slew rate, output offset and open loop gain for opamp.
- Ques 2 A]** Attempt any **TWO** of the following – [6]
- a) State two advantages and one *disadvantage* of BR over FWR.
- b) Explain simplex and duplex communication systems using one example each.
- c) Explain using circuit diagram, the working of *any one* type of comparator using IC741 as opamp.
- B]** Attempt any **ONE** of the following – [4]
- a) Explain the working of speaker transducer with neat diagram.
- b) Explain the working of FWR with circuit. Draw input and output waveforms.
- Ques 3 : A]** Attempt any **TWO** of the following - [6]
- a) How the opamp can be used as integrator? Derive output equation with circuit diagram.
- b) Draw the block diagram of digital multimeter and explain its working.
- c) Explain with the help of diagram working of LAN as star and ring networks.
- B]** Attempt any **ONE** of the following – [4]
- a) Draw the block diagram of CRO, and explain the function of each block.
- b) What is LVDT? Explain its working with block diagram.
- Ques 4 A]** Attempt any **TWO** of the following – [6]
- a) Draw circuit diagram of two transistors regulator circuit and explain its working.
- b) Explain piezo electric transducer in brief.
- c) Draw circuit diagram of non-inverting amplifier and derive its output expression.
- B]** Attempt any **ONE** of the following – [4]
- a) Derive the output equation of AM wave and draw its diagram.
- b) Draw the block diagram of optical fiber communication system.
- Ques 5 A]** Attempt any **TWO** of the following – [6]
- a) Define FM and give its properties with diagram.
- b) Write a short note on capacitive transducer.
- c) Explain the working of differential amplifier with diagram. What is CMRR?.
- B]** Attempt any **ONE** of the following – [4]
- a) Draw the internal block diagram of opamp and explain the function of each block.
- b) Design voltage regulator using IC LM 317 for $V_o = 10V$, (if $V_{ref} = 1.25V$) and $R_1 = 5k\Omega$.
- OR**
- Ques 5 A]** Attempt any **TWO** of the following – [6]
- a) Draw the circuit of opamp as an adder and find V_o if $V_1 = 2mV$, $V_2 = 5mV$ and $V_3 = 7mV$, consider that $R_1 = R_2$.
- b) Draw the block diagram of IC 555 and explain its working.
- c) How capacitive filter circuit works? Explain with diagram.
- B]** Attempt any **ONE** of the following – [4]
- a) What are the elements of communication system? Explain with diagram and example.
- b) Define LR and SR for a DC power supply with an example of each.





- Ques 1 : A]** Select correct alternative and rewrite the sentence : [4]
- a] The binary value of $(111100110111.101100000001)_2$ will be _____.
(F37.B01)₁₆, (F37.110)₁₆, (E47.C01)₁₆, (101.B01)₁₆
- b] When any one input of Ex-OR gate is at logic-1, the circuit works as _____.
NOR gate, NAND gate, NOT gate, Ex-OR gate
- c] The number of flip-flops required for MOD-30 counter will be _____.
Nine, five, seven, sixty-four
- d] For constructing an OR gate using NOR gates, the number of NOR gates required will be _____.
2, 5, 3, 1

- B]** Attempt any **TWO** of the following – [6]
- a] Explain the working of simultaneous type AD converter circuit using diagram.
b] What is encoder? Explain decimal to BCD encoder with necessary logic diagram.
c] Why NAND gate is called UBB? Explain how it can be used to construct basic gates.

- Ques 2 A]** Attempt any **TWO** of the following – [6]
- a] Explain double-dabble method with any one example.
b] Draw the block diagram of basic computer and explain its three sections.
c] Convert the given numbers into binary: $(36.25)_{10}$, $(108.45)_{10}$, $(263.8)_{10}$

- B]** Attempt any **ONE** of the following – [4]
- a] Draw the circuit of 4:1 line mux and explain its working with output equation and truth table.
b] In a circuit of 4-bit R-2R ladder find: (a) full scale output (b) for input 0110, if $0 = 0V$ and $1 = 16V$.

- Ques 3 : A]** Attempt any **TWO** of the following – [6]
- a] Mention the names of basic memories used in computer.
b] Draw the circuit of CMOS NOR gate and explain its working.
c] What is controlled inverter? Explain its working.

- B]** Attempt any **ONE** of the following – [4]
- a] What is a demultiplexer? Design 1:4 Mux using gates and explain its working.
b] State and prove De Morgan's both theorems.

- Ques 4: A]** Attempt any **TWO** of the following – [6]
- a] Draw the circuit of M/S flip-flop and explain its working.
b] Draw the circuit of 1:16 line demux with detailed labels.
c] Explain the working of right shift register using circuit diagram.

- B]** Attempt any **ONE** of the following – [4]
- a] Draw the circuit of asynchronous counter and explain its working with wave diagrams.
b] Draw the circuit of full adder and explain its working.

- Ques 5 A]** Attempt any **TWO** of the following – [6]
- a] Mention the classification of logic families.
b] What is encoder? Explain its working and draw its logic diagram also.
c] Define basic gates with circuit diagram and truth tables.

- B]** Attempt any **ONE** of the following – [4]
- a] Define: fan out, figure of merit, power dissipation, propagation delay.
b] Discuss the working of 4-bit binary adder using circuit diagram.

OR

- Ques 5 A]** Attempt any **TWO** of the following – [6]
- a] Explain the process of SAR with circuit diagram.
b] Subtract $(36)_{10}$, from $(43)_{10}$, using 2's complement method and obtain the answer in binary.
c] What is decoder? Explain its working with suitable diagram.

- B]** Attempt any **ONE** of the following - [4]
- a] Compare TTL and CMOS logic circuits with any four points.
b] Prove the following identities –

$$1) (\bar{A} + B + C)(A + \bar{B} + C)(A + B + \bar{C}) = AB + BC + AC + \bar{A}.\bar{B}.\bar{C}$$

$$2) (\bar{A} + B)(\bar{B} + C)(A + \bar{C}) = ABC + \bar{A}.\bar{B}.\bar{C}$$

The End