


# Basic Gates (Slip-1)

## HSC Board Questions Slip (Study of logic gates)


- You are given ICs \_\_\_\_\_, \_\_\_\_\_, \_\_\_\_\_.
- Identify them and draw their pin configurations. Write their typical specifications. (5)
  - Draw the circuit diagram for testing the logic gates. (5)
  - Connect the circuit and get it checked by the examiner. (5)
  - Determine the phase difference between two signals by calculations. (5)
  - Compare the theoretical and practical values by tabulating them. (5)
  - Oral (5)



### Circuit diagrams –

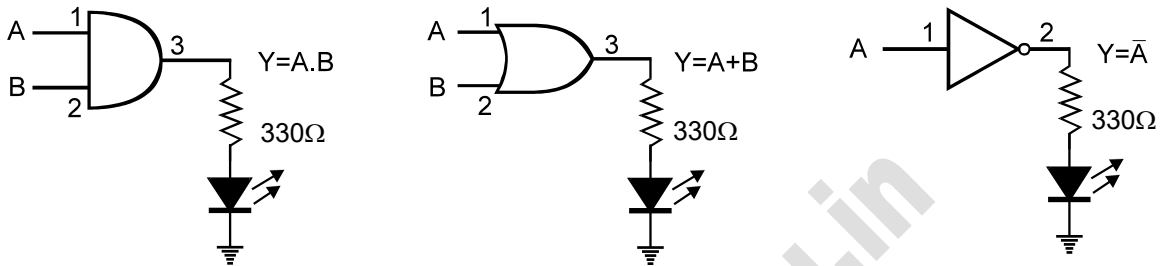

### Pin configurations of the ICs –

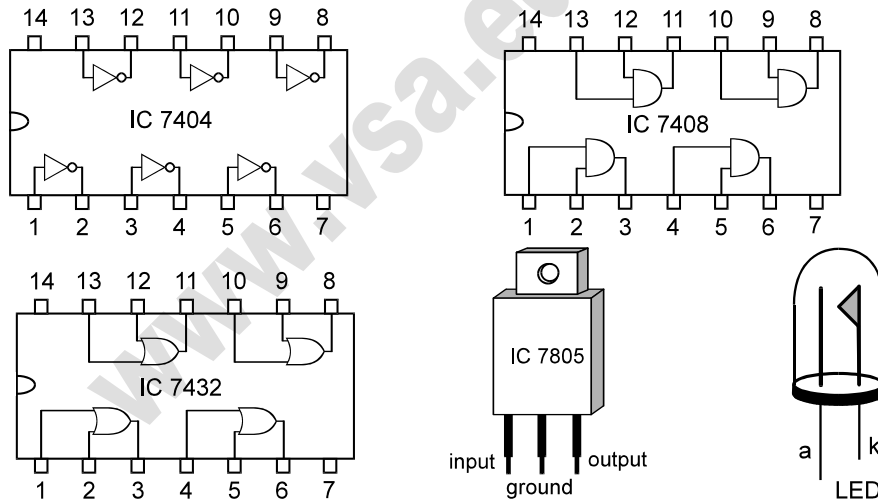

### Specifications of components –

Type of component	Specifications
IC 7404	Hex inverter, NOT gate
IC 7408	Quad 2-input AND gate
IC 7432	Quad 2-input OR gate
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, 1/4W, carbon composition, ±5% tolerance
LED	color _____, VF = _____
Diodes	1N4001 rectifier diode
Capacitor	1000μF/25V electrolytic capacitor
Transformer	6V–0V–6V, 500mA secondary transformer

# De Morgan's theorems (Slip-2)







## HSC Board Questions Slip (Study of De Morgan's Theorems)

- You are given ICs \_\_\_\_\_, \_\_\_\_\_, \_\_\_\_\_.
- Identify them and draw their pin configurations. Write their typical specifications. (5)
  - State De Morgan's theorems and draw the circuit diagram for verifying them. (5)
  - Connect the circuits and show them to the examiner. (5)
  - Test the outputs for various combinations of inputs. Tabulate the results. (5)
  - Compare experimentally observed results and expected results. (5)
  - Oral (5)








### Circuit diagrams –

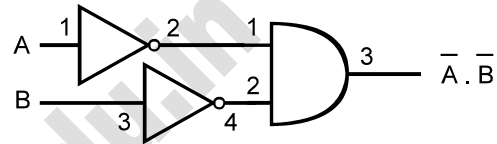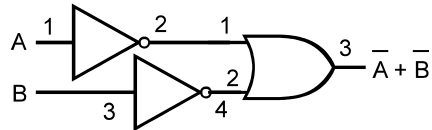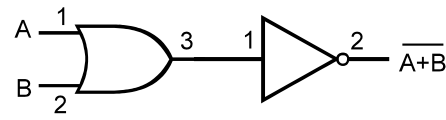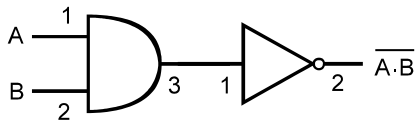

NAND gate is equivalent to bubbled OR gate

NOR gate is equivalent to bubbled AND gate

### Pin configurations of the ICs –

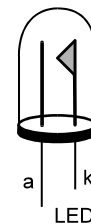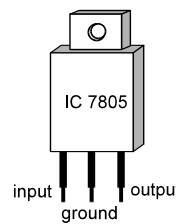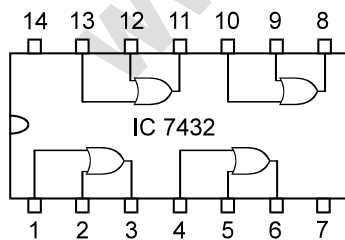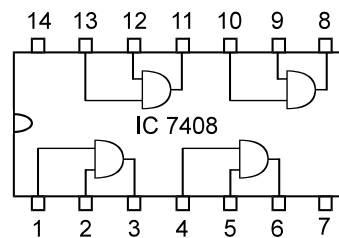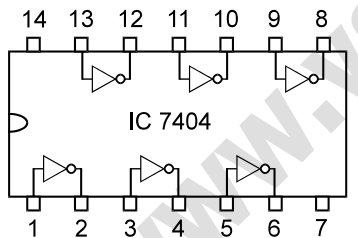

### Specifications of components –

Type of component	Specifications
IC 7404	Hex inverter, NOT gate
IC 7408	Quad 2-input AND gate
IC 7432	Quad 2-input OR gate
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, 1/4W, carbon composition, ±5% tolerance
LED	color _____, VF = _____
Diodes	1N4001 rectifier diode
Capacitor	1000μF/25V electrolytic capacitor
Transformer	6V–0V–6V, 500mA secondary transformer

# Universal Building Blocks (Slip-3)




## HSC Board Questions Slip (Study of Universal Building Blocks)


- You are given ICs \_\_\_\_\_, \_\_\_\_\_.
- Identify them and draw their pin configurations. Write their typical specifications. (5)
  - Draw the circuit diagram for constructing the basic gates using NAND/NOR gates. (5)
  - Connect the circuit and get it checked by the examiner. (5)
  - Switch on circuit and check its output for different combinations of inpts. Draw TTs. (5)
  - Compare the theoretical and practical values in tabular form. (5)
  - Oral (5)



### Circuit diagrams –

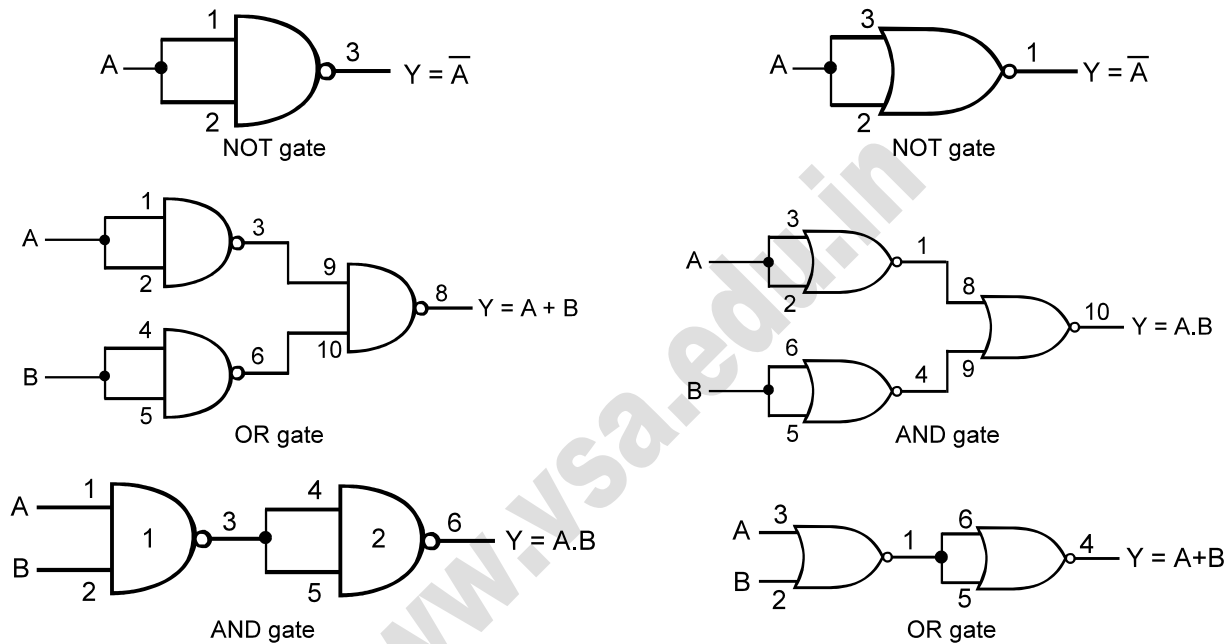

### Pin configurations of the ICs –

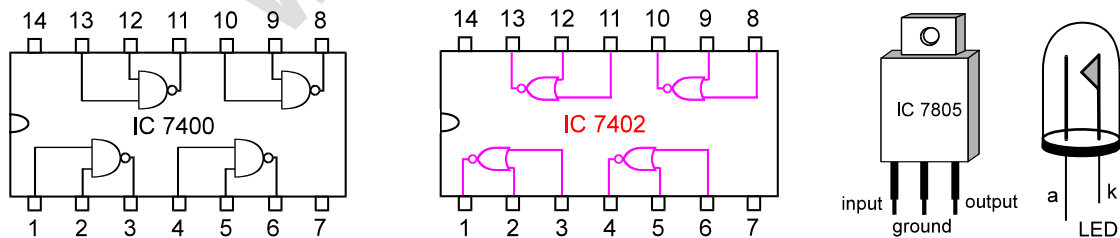

### Specifications of components –

Type of component	Specifications
IC 7400	Quad 2-input NAND gate
IC 7402	Quad 2-input NOR gate
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, 1/4W, carbon composition, ±5% tolerance
LED	color _____, V <sub>F</sub> = _____
Diodes	1N4001 rectifier diode
Capacitor	1000μF/25V electrolytic capacitor
Transformer	6V–0V–6V, 500mA secondary transformer

# Boolean Equations (Slip-4)

## HSC Board Questions Slip (Study of Boolean Equations)

You are given with the Boolean equation → \_\_\_\_\_


- Draw the logic diagram for given logic equation and list the gates required. (5)
- Reduce the equation using Boolean laws and again draw the logic diagram. (5)
- List the ICs required, give their pin configurations and specifications. (5)
- Connect the circuit and test it. (5)
- Verify output of circuit by comparing experimental & expected results. Tabulate them. (5)
- Oral (5)

### Circuit diagram –

The student must draw the circuit diagram of given equation.  
For this experiment, circuit diagram will NOT be supplied.



### Pin configurations of basic ICs –

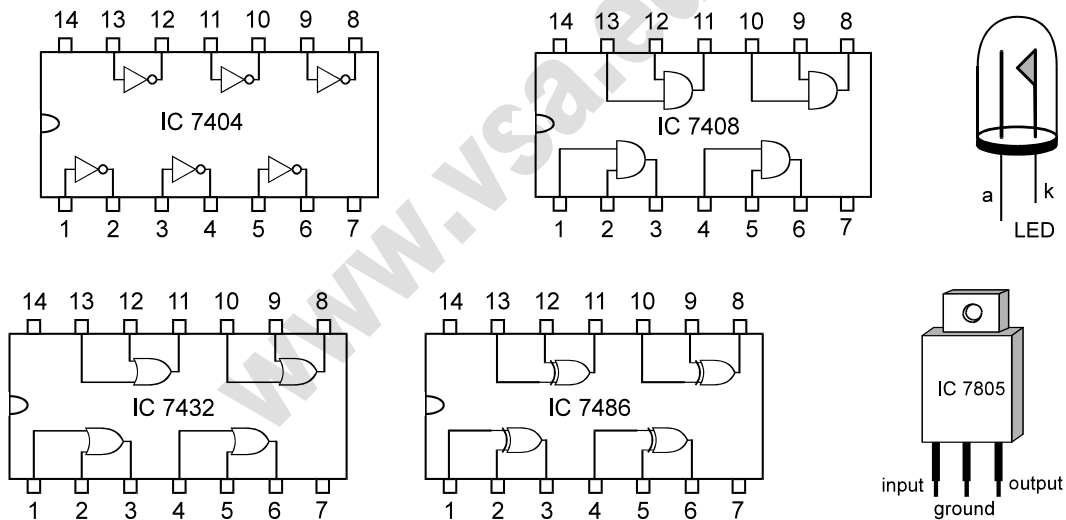

### Specifications of components –

Type of component	Specifications
IC 7404	Hex inverter, NOT gate
IC 7408	Quad 2-input AND gate
IC 7432	Quad 2-input OR gate
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, 1/4W, carbon composition, ±5% tolerance
LED	color _____, VF = _____
Diodes	1N4001 rectifier diode
Capacitor	1000μF/25V electrolytic capacitor
Transformer	6V–0V–6V, 500mA secondary transformer

# Ex-OR gate using Basic gates (Slip-5)




## HSC Board Questions Slip (Study of Ex-OR gate)






You are given ICs: IC 7408, IC 7432 and IC 7404.

- a) Identify them. (3)      b) Define Ex-OR logic. (1)      c) Write TT of Ex-OR gate. (1)
- d) Draw the logic diagram of Ex-OR gate using basic gates and connect the circuit. (10)
- e) Verify working of circuit constructed by you as per TT. (3)
- f) Convert it to Ex-NOR and again test the circuit. (2)      g) Test IC 7486. (5)
- h) Oral (5)

### Circuit diagram –

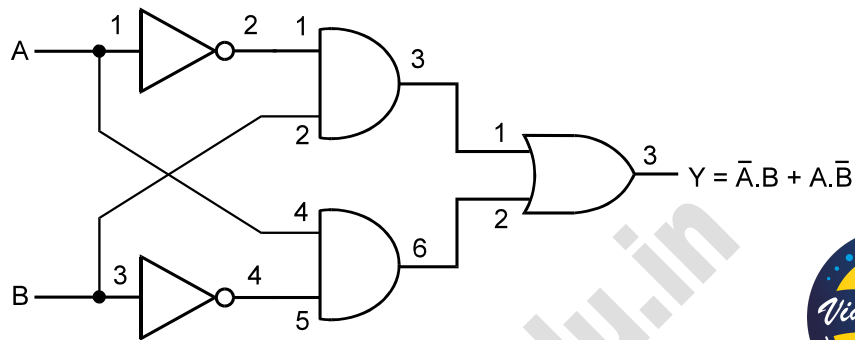

### Pin configurations of ICs –

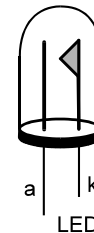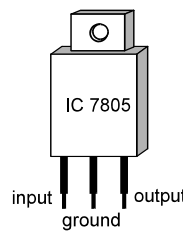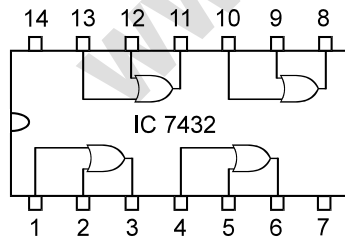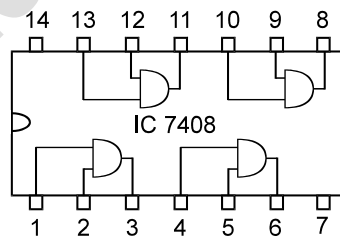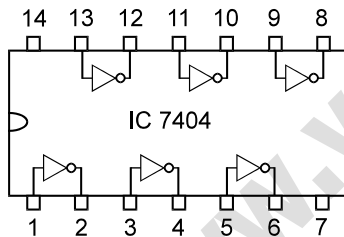

### Specifications of components –

Type of component	Specifications
IC 7404	Hex inverter, NOT gate
IC 7408	Quad 2-input AND gate
IC 7432	Quad 2-input OR gate
IC 7486	Quad 2-input Ex-OR gate
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, 1/4W, carbon composition, ±5% tolerance
LED	color _____, VF = _____
Diodes	1N4001 rectifier diode
Capacitor	1000μF/25V electrolytic capacitor
Transformer	6V-0V-6V, 500mA secondary transformer

# Ex-OR gate using NAND gates (Slip-6)




## HSC Board Questions Slip (Study of Ex-OR gate)




You are given ICs: IC 7400 and IC 7486.

- b) Identify them and draw their pin diagrams showing the layout of gates. (4)
- c) Define Ex-OR logic. (1)
- d) Draw logic diagram of Ex-OR gate using NAND gates. How will you convert it to Ex-NOR? Draw the circuit again. (5)
- e) Connect the circuit of Ex-OR using NAND gates and verify the output as per TT. (10)
- f) Test IC 7486 separately. (5)
- g) Oral (5)

### Circuit diagram –

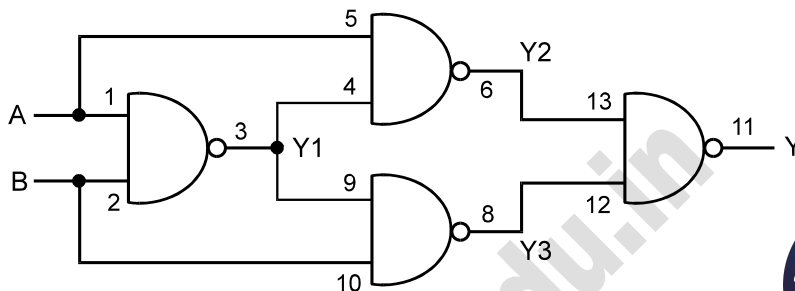

### Pin configurations of ICs –

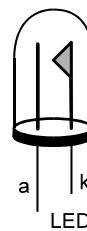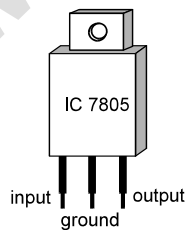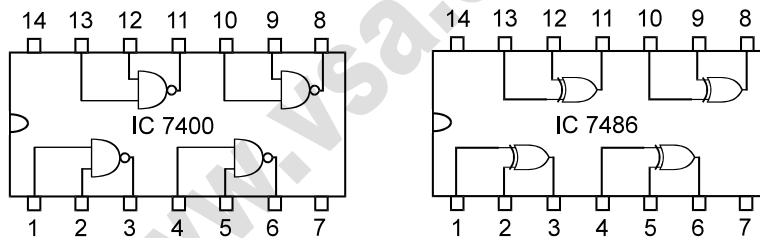

### Specifications of components –

Type of component	Specifications
IC 7400	Quad 2-input NAND gate
IC 7486	Quad 2-input Ex-OR gate
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, ¼W, carbon composition, ±5% tolerance
LED	color _____, VF = _____
Diodes	1N4001 rectifier diode
Capacitor	1000µF/25V electrolytic capacitor
Transformer	6V-0V-6V, 500mA secondary transformer

# Controlled Inverter (Slip-7)




## HSC Board Questions Slip (Study of controlled inverter using Ex-OR)




You are given IC 7486.

- h) Identify the IC and draw its pin configuration. (5)
- i) Draw the circuit diagram of a 4-bit controlled inverter. (5)
- j) Write the working of 4-bit controlled inverter and mention its one application. (5)
- k) Connect the circuit of controlled inverter. (5)
- l) Demonstrate the working of your circuit for any two 4-bit binary numbers and note down the input and output numbers. Write their result and show it to examiner. (5)
- m) Oral (5)

### Circuit diagram –

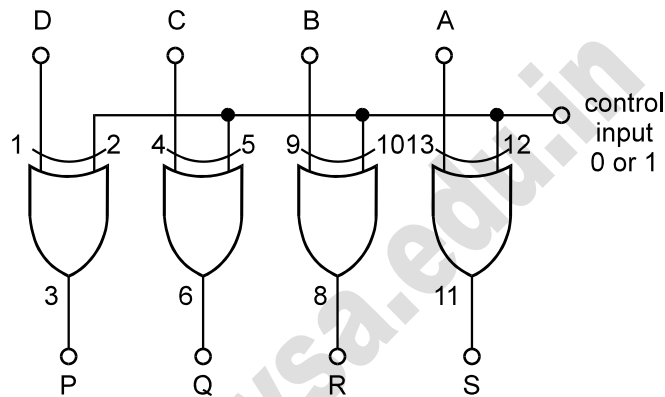

### Pin configurations of ICs –

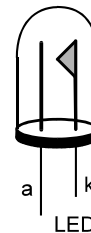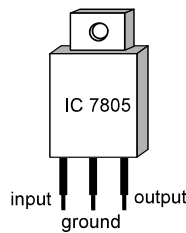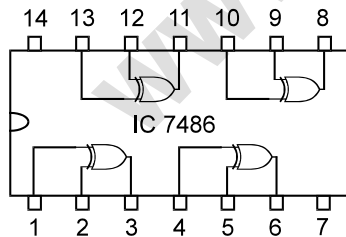

### Specifications of components –

Type of component	Specifications
IC 7486	Quad 2-input Ex-OR gate
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, 1/4W, carbon composition, ±5% tolerance
LED	color _____, V <sub>F</sub> = _____
Diodes	1N4001 rectifier diode
Capacitor	1000μF/25V electrolytic capacitor
Transformer	6V-0V-6V, 500mA secondary transformer


# Noise Margin (Slip-8)

## HSC Board Questions Slip (Study of controlled inverter using Ex-OR)


You are given IC 7404.

- n) Write its specifications and pin diagram. (5)
- o) Draw the circuit arrangement for determination of input and output voltage characteristics. (5)
- p) Measure the output voltages for different input voltages starting from 0Volts to 1.5Volts. Tabulate the readings (at least 15 readings). (5)
- q) Measure source current, sink current and output voltage for various loads (by connecting different number of NOT gates to output i.e. one to five NOT gates, tabulate the readings). (5)
- r) Oral (5)

### Circuit diagrams –

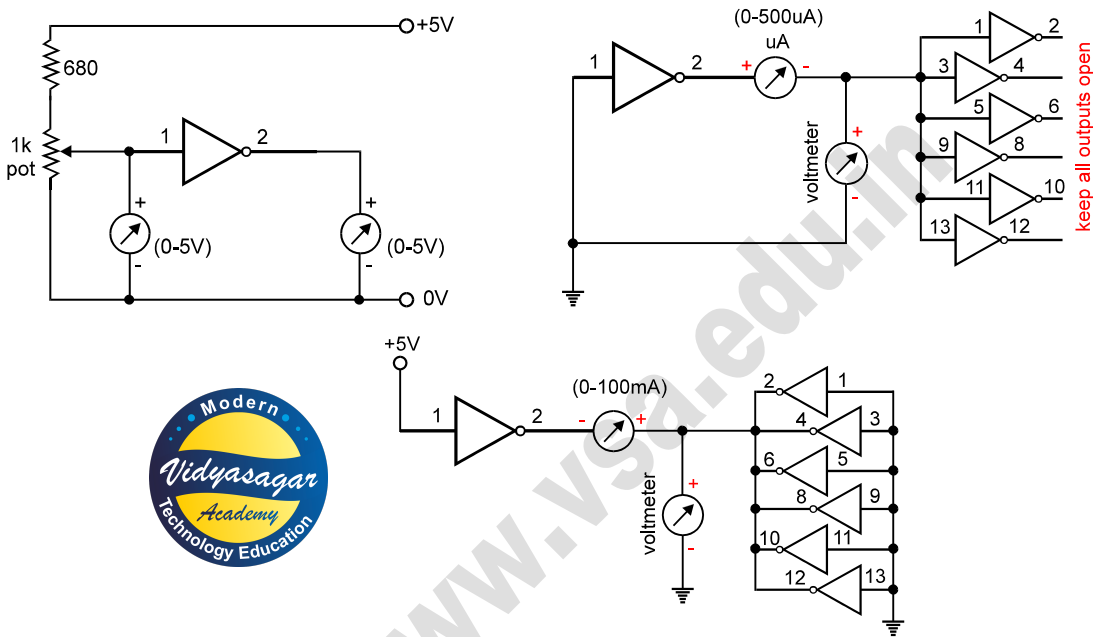

### Pin configurations of ICs –

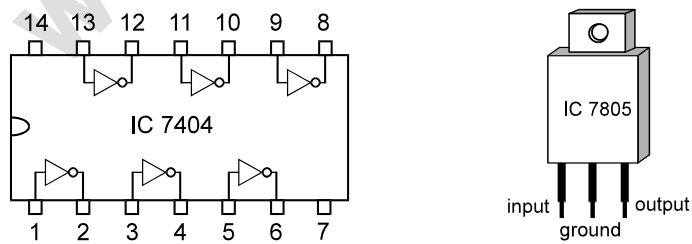

### Specifications of components –

Type of component	Specifications
IC 7404 (2 Nos.)	Hex inverter, NOT gate
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, ¼W, carbon composition, ±5% tolerance
LED	color _____, VF = _____
Diodes	1N4001 rectifier diode
Capacitor	1000µF/25V electrolytic capacitor
Transformer	6V-0V-6V, 500mA secondary transformer



# RS FF using NAND/NOR gates (Slip-9)



## HSC Board Questions Slip (Study of RS FF using NAND & NOR gates)


You are given IC 7400 and 7402.

- s) Identify the IC and draw its pin specifications. (2)
- t) Draw circuit diagram of RS FF using NAND gates and write its TT. (5)
- u) Construct the circuit and verify the truth table. (5)
- v) Draw circuit diagram of RS FF using NOR gates and write its TT. (5)
- w) Construct the circuit and verify the truth table. (5)
- x) Compare the TTs of RS FF using NAND and NOR gates and write the difference. (3)
- y) Oral (5)

### Circuit diagrams –



### Pin configurations of the ICs –

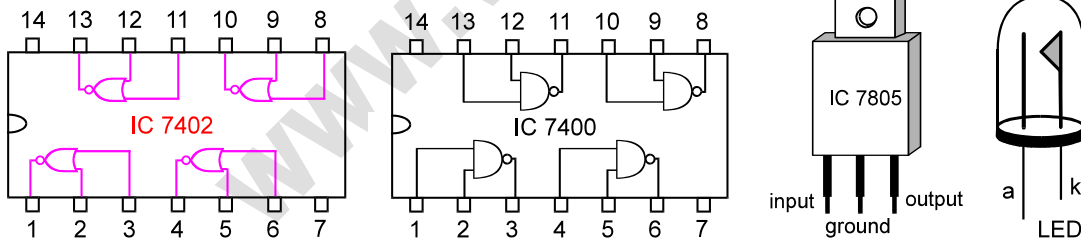

### Specifications of components –

Type of component	Specifications
IC 7400	Quad 2-input NAND gate
IC 7402	Quad 2-input NOR gate
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, 1/4W, carbon composition, ±5% tolerance
LED	color _____, VF = _____
Diodes	1N4001 rectifier diode
Capacitor	1000μF/25V electrolytic capacitor
Transformer	6V–0V–6V, 500mA secondary transformer


# Decoder (Slip-13)

## HSC Board Questions Slip (Study of Decoder)


You are given IC 7447/IC 7448 with 7-segment display.

- z) Identify the ICs and draw their specifications. (5)
- aa) Draw the circuit diagram for testing the above ICs. (5)
- bb) Connect it to obtain different digits for different BCD inputs. (5)
- cc) Test the circuit for different input conditions. (5)
- dd) Tabulate the observations. (5)
- ee) Oral (5)

### Circuit diagrams –

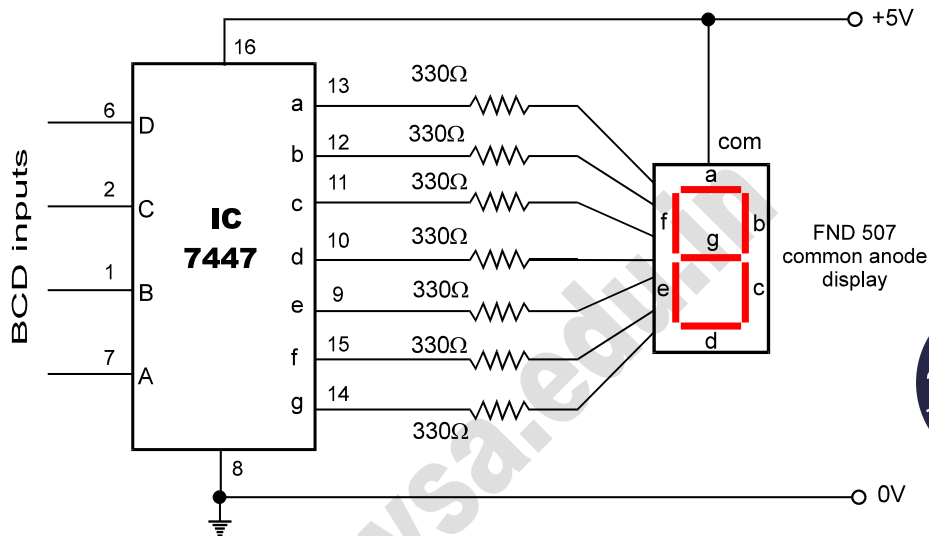

### Pin configurations –

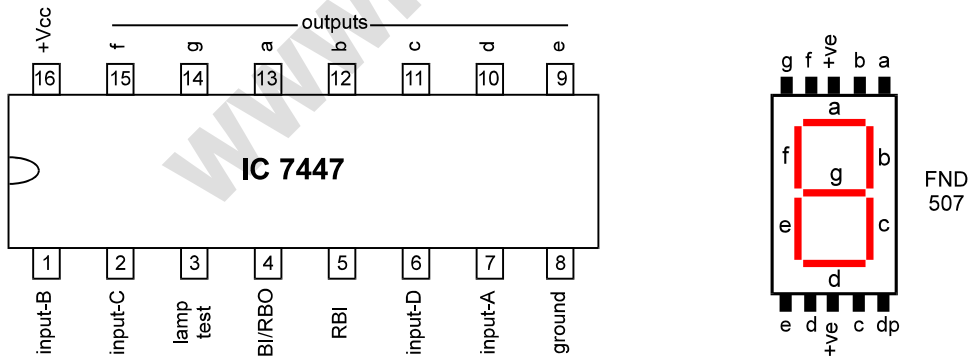

### Specifications of components –


Type of component	Specifications
IC 7447	14-pin, BCD to 7-segment decoder/driver TTL IC
FND 507	color _____, VF of LED segment = _____
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, ¼W, carbon composition, ±5% tolerance
Diodes	1N4001 rectifier diode
Capacitor	1000µF/25V electrolytic capacitor
Transformer	6V–0V–6V, 500mA secondary transformer

# Half Adder (Slip-15)




## HSC Board Questions Slip (Study of half adder)

- ff) Draw the logic diagram of half adder using logic gates. (5)
- gg) List the number of ICs required, write their specifications and pin configurations. (5)
- hh) Construct the circuit on the given board. (5)
- ii) Test the circuit for all possible input combinations. (5)
- jj) Tabulate the results. (5)
- kk) Oral (5)

### Circuit diagram –

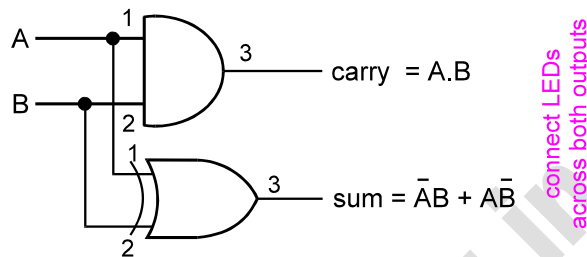

### Pin configurations of ICs –

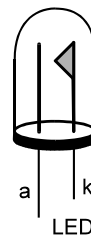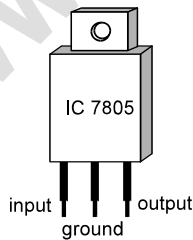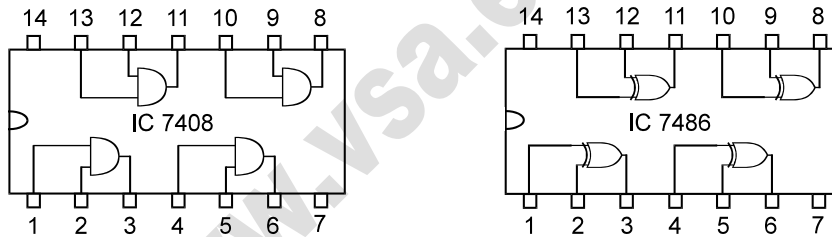

### Specifications of components –

Type of component	Specifications
IC 7408	Quad 2-input AND gate
IC 7486	Quad 2-input Ex-OR gate
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, ¼W, carbon composition, ±5% tolerance
LED	color _____, VF = _____
Diodes	1N4001 rectifier diode
Capacitor	1000µF/25V electrolytic capacitor
Transformer	6V–0V–6V, 500mA secondary transformer


# Full Adder (Slip-16)

## HSC Board Questions Slip (Study of full adder)


- ll) Draw the logic diagram of full adder using logic gates. (5)
- mm) List the number of ICs required, write their specifications and pin configurations. (5)
- nn) Construct the circuit on the given board. (5)
- oo) Test the circuit for all possible input combinations. (5)
- pp) Tabulate the results. (5)
- qq) Oral (5)



### Circuit diagram –

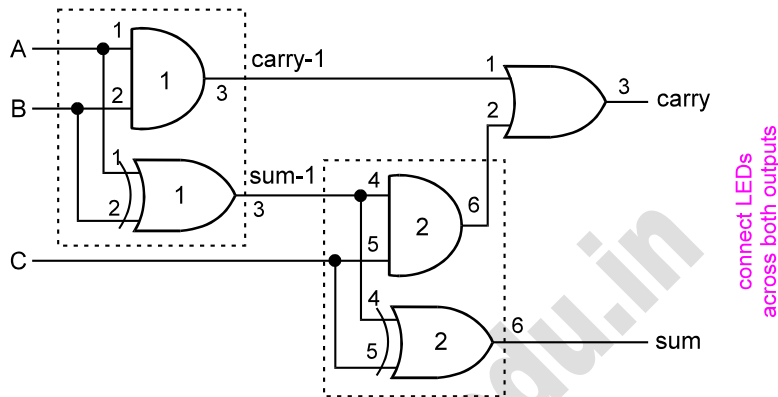

### Pin configurations of ICs –

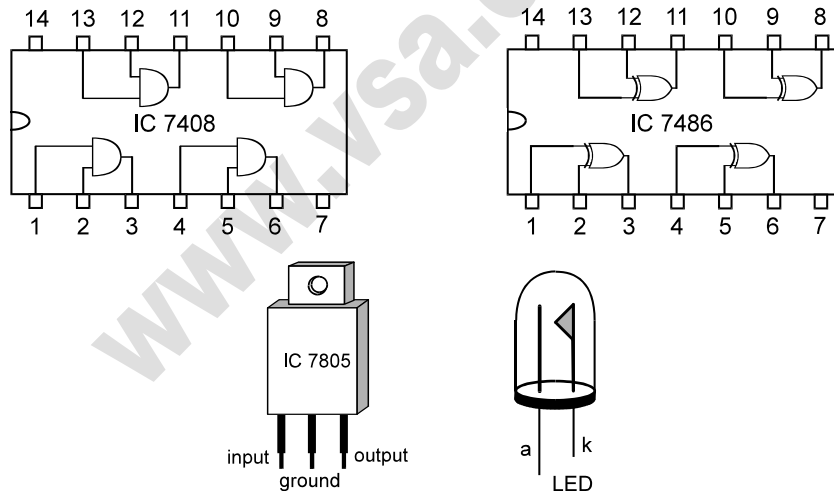

### Specifications of components –

Type of component	Specifications
IC 7408	Quad 2-input AND gate
IC 7486	Quad 2-input Ex-OR gate
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, 1/4W, carbon composition, ±5% tolerance
LED	color _____, VF = _____
Diodes	1N4001 rectifier diode
Capacitor	1000μF/25V electrolytic capacitor
Transformer	6V–0V–6V, 500mA secondary transformer


# 4-bit Binary Adder (Slip-17)




## HSC Board Questions Slip (study of 4-bit binary adder)

- rr) You are given IC 7483. Identify the IC and write its specifications. Draw pin configuration. (5)
- ss) Construct the circuit for addition of two 4-bit binary numbers. (5)
- tt) Add following number after converting into their binary equivalents and verify the results. (10)  
 $( )_{10} + ( )_{10}, ( )_{10} + ( )_{10}, ( )_{10} + ( )_{10}, ( )_{10} + ( )_{10}, ( )_{10} + ( )_{10}$
- uu) How can this circuit be used for 4-bit binary subtraction? Draw the circuit diagram. (5)
- vv) Oral (5)

### Circuit diagram –

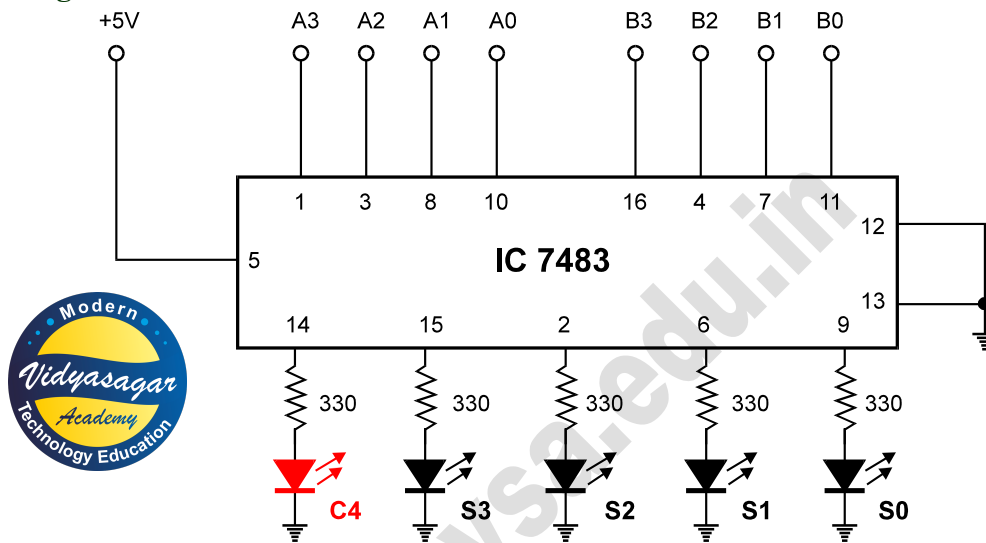

### Pin configurations –

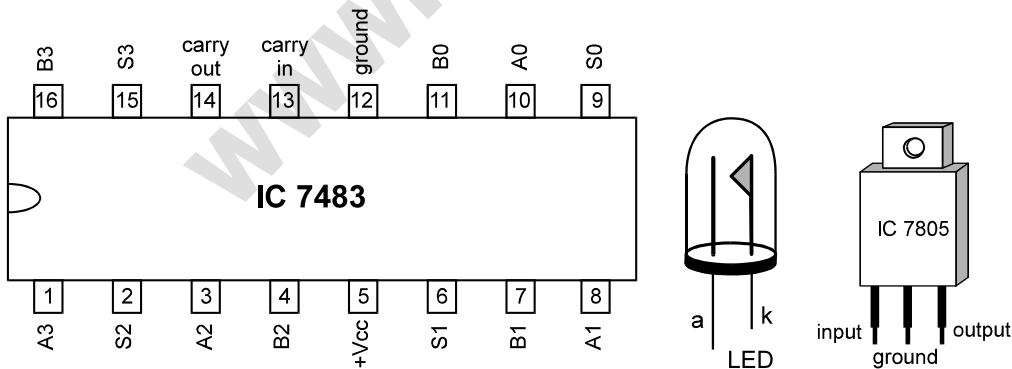

### Specifications of components –

Type of component	Specifications
IC 7483	4-bit full adder TTL IC, supply voltage = 5V, 16 pins IC
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, 1/4W, carbon composition, ±5% tolerance
LED	color _____, VF = _____
Diodes	1N4001 rectifier diode
Capacitor	1000μF/25V electrolytic capacitor
Transformer	6V–0V–6V, 500mA secondary transformer


# Schmitt Trigger Inverter (Slip-18)




## HSC Board Questions Slip (Schmitt trigger inverter)

- ww) You are given IC 7414. Identify IC and write its specifications. Draw pin configuration. (5)
- xx) Draw the circuit diagram of square wave generator using above IC. (5)
- yy) Write the expression for the period of output waveform. Calculate the values of R & C for three different frequencies. Draw the ideal output voltage waveform of the circuit. (5)
- zz) Connect the circuit for different values of R & C. Observe the waveforms on CRO. (5)
- aaa) Measure the periods and frequencies and compare them with theoretical values. (5)
- bbb) Oral. (5)

### Circuit diagram –

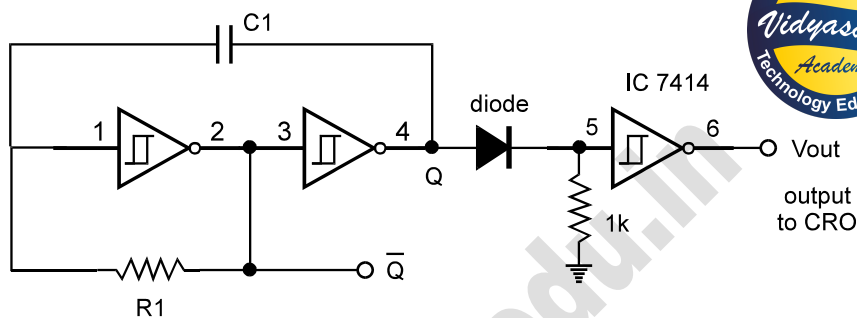

### Pin configurations of the ICs –

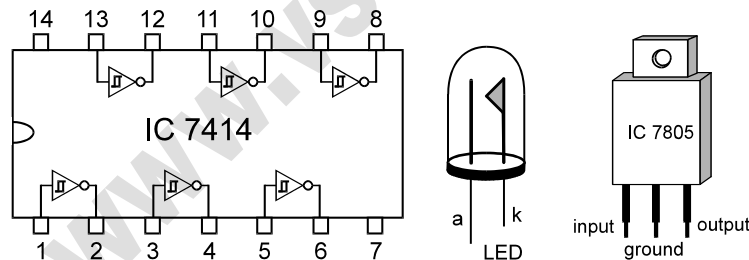

### Specifications of components –

Type of component	Specifications
IC 7414	Schmitt trigger hex inverter, TTL IC
IC 7805	+5V, 3-terminal regulator IC
Resistors	330Ω, 1/4W, carbon composition, ±5% tolerance 1kΩ, 1/4W, carbon composition, ±5% tolerance 220Ω, 1/4W, carbon composition, ±5% tolerance 180Ω, 1/4W, carbon composition, ±5% tolerance
Diodes	1N4001 rectifier diode
Capacitors	1000μF/25V electrolytic filter capacitor 0.1μF/32V, ceramic capacitor 0.2μF/32V, ceramic capacitor 0.05μF/32V, ceramic capacitor
Transformer	6V–0V–6V, 500mA secondary transformer




# D/A Converter (Slip-20)


## HSC Board Questions Slip (Digital to Analog Converter)

- iii) Draw the circuit diagram of 4-bit D/A converter using R-2R ladder (use opamp at output). (5)
- jjj) Assemble the circuit. (5)
- kkk) Observe the output for the binary inputs  $\rightarrow$  ( ), ( ), ( ), ( ) (5)
- lll) Calculate the output for the above binary inputs. (5)
- mmm) Compare the calculated and observed values. (5)
- nnn) Oral. (5)

### Circuit diagram –

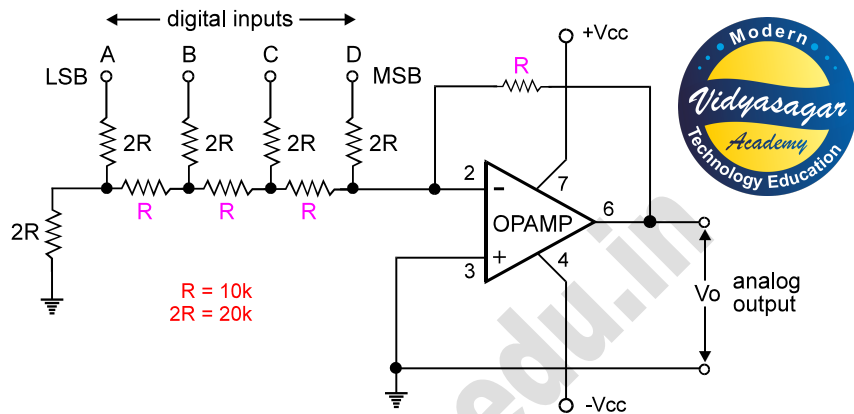

### Pin configurations of the IC –

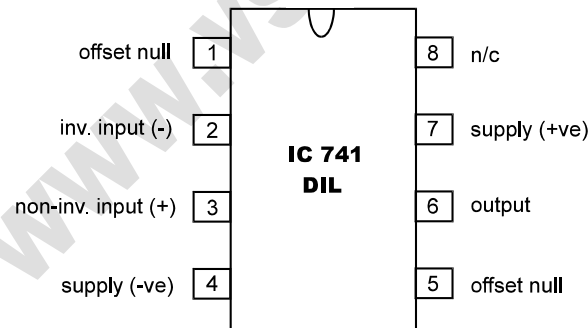

### Specifications of components –

Type of component	Specifications
IC 741	Operational amplifier, 8 pins, $\pm 18V$ max dual power supply
IC 7812	+12V, 3-terminal regulator IC
IC 7912	-12V, 3-terminal regulator IC
Resistors	10k $\Omega$ , 1/4W, carbon composition, $\pm 5\%$ tolerance 330 $\Omega$ , 1/4W, carbon composition, $\pm 5\%$ tolerance
Potentiometer	1k $\Omega$ , linear potentiometer
Diodes	1N4001 rectifier diode
Capacitors	1000 $\mu F$ /25V electrolytic filter capacitor
Transformer	9V-0V-9V, 500mA secondary transformer



# Diode Matrix ROM (Slip-21)



## HSC Board Questions Slip (Diode Matrix ROM)

ooo) Draw the circuit for 4 x 4 diode matrix ROM, for the following 4-bit words –

Location content of words –


0 → (            )<sub>2</sub>, 1 → (            )<sub>2</sub>, 2 → (            )<sub>2</sub>, 3 → (            )<sub>2</sub>, (7)

ppp) Assemble the circuit. (8)


qqq) Test and verify the output for various locations. (10)

rrr) Oral. (5)

### Circuit diagram –

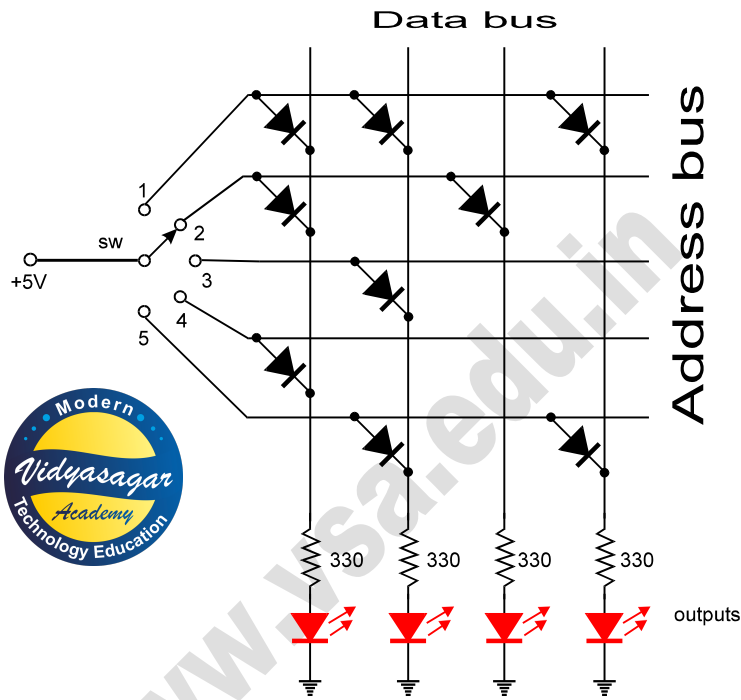

### Pin configurations –

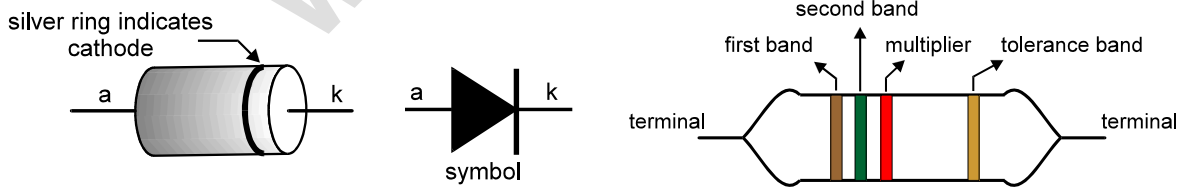

### Specifications of components –

Type of component	Specifications
Resistors	10kΩ, ¼W, carbon composition, ±5% tolerance 330Ω, ¼W, carbon composition, ±5% tolerance
Potentiometer	1kΩ, linear potentiometer
Diodes	1N4001 rectifier diode
LEDs	color _____, VF = _____
Capacitors	1000µF/25V electrolytic filter capacitor
Transformer	9V–0V–9V, 500mA secondary transformer
Rotary switch	1–pole, 5–way rotary switch