

Guessing Paper March 2022
Applied Electronics Paper-1

Time: 3 Hrs.

Std. XII Electronics

Marks: 50

Ques 1 A] Fill in the blanks by choosing the *correct* alternative –

- a] The average dc voltage of BR is _____. [1]
1] $2\pi/V_p$
2] $2V_p/\pi$
3] V_p/π
4] $2V_p \times \pi$
- b] When negative voltage on control grid is increased, _____ of screen drops. [1]
1] focus
2] brightness
3] color
4] None of the above
- c] The opamp can amplify _____. [1]
1] dc signals only
2] ac signals only
3] ac/dc signals
4] weak dc signals only
- d] _____ multivibrator is an oscillator. [1]
1] Bistable
2] Monostable
3] Astable
4] One-shot

B] Attempt any **TWO** of the following: [6]

- a] Draw the block diagram of CRO and explain its function of each block.
b] In HWR, if transformer secondary AC voltage is $12V_{rms}$ and load resistance is 100Ω , then calculate V_{dc} , I_{dc} , V_p and PIV of the diode.
c] Explain the working of gas sensor with diagram.

Ques 2 A] Attempt any **TWO** of the following – [6]

- a] Draw the circuit of inverting amplifier using opamp and derive its output equation.
b] What is RADAR? Explain how the distance of target is measured using RADAR.
c] In an IC 555 timer if $R = 1M\Omega$ and $C = 100\mu F$, find its time delay (T).

B] Attempt any **ONE** of the following – [4]

- a] Explain any two types of applications of satellite in brief.
b] Draw block diagram of opamp and explain its working block-by-block.

Ques 3 : A] Attempt any **TWO** of the following - [6]

- a] Find the output voltage for an inverting adder, if $R_1 = R_2 = R_3 = 2k\Omega$ and $R_f = 10k\Omega$, with input voltages are $-1V$, $3V$ and $7V$.
b] Draw the block diagram of digital multimeter and explain its working.
c] Explain with the help of suitable diagram principle working of cellular radio system.

B] Attempt any **ONE** of the following – [4]

- a] Explain the use of CRO in (a) AC voltage measurement (b) DC current measurement.
b] A FWR is connected to a transformer of turns ratio 50:15. Find its average DC voltage (V_{dc}), PIV and ripple frequency, if input voltage is $200V_{rms}$ AC, 50Hz.

Ques 4 A] Attempt any **TWO** of the following – [6]

- a) Draw circuit diagram of two transistors regulator circuit and explain its working.
- b) Explain piezo electric transducer in brief.
- c) Draw circuit diagram of inverting integrator and derive its output expression.

B] Attempt any **ONE** of the following – [4]

- a) Draw block diagram of CRO and explain its working.
- b) Derive the expression for amplitude modulated wave.

Ques 5 A] Attempt any **TWO** of the following – [6]

- a) How opamp is used as a subtractor? Draw a circuit diagram for it.
- b) Explain capacitive input filter circuit with diagram.
- c) Draw pin diagram of IC 741 and state function of each pin.

B] Attempt any **ONE** of the following – [4]

- a) What are the criteria to select a transducer for a system?
- b) Explain the frequency response curve of an opamp with graph.

OR

Ques 5 A] Attempt any **TWO** of the following – [6]

- a) What is half and full duplex communication system? Explain.
- b) Draw block diagram of 3-terminal IC regulator circuit and explain its working.
- c) Define the following –
 - a) Slew rate
 - b) Open loop gain
 - c) Closed loop gain

B] Attempt any **ONE** of the following – [4]

- a) Draw block diagram of IC 555 and explain its working.
- b) Compare the AM & FM processes with any four points.

The End

Guessing Paper March 2022
Digital Electronics Paper-2

Time: 3 Hrs.

Std. XII Electronics

Marks: 50

Ques 1 : A] Select correct alternative and rewrite the sentence :

- a]** The property of flip-flop to hold the stored information is called _____. [1]
1] Resetting of flip-flop
2] Setting of flip-flop
3] Memory
4] None of these
- b]** The bubbled OR gate is equivalent to _____. [1]
1] NOT gate
2] NAND gate
3] AND gate
4] Ex-OR gate
- c]** A multiplexer circuit with 8 inputs will have _____ select inputs. [1]
1] Five
2] Three
3] Twenty four
4] None of these
- d]** A 48kHz clock signal can be reduced to 8kHz using _____ counter. [1]
1] MOD-14 counter
2] MOD-6 counter
3] MOD 10 counter
4] None of the above

B] Attempt any TWO of the following – [6]

- a]** Convert the following –
(a) $[1FD5]_{16} = [?]_2$ (b) $[1010101.011010010]_2 = [?]_{16}$ (c) $[27.F04]_{16} = [?]_{10}$
- b]** Calculate output state of 3-bit counter, when it receives 23rd clock pulse. Initially its output starts from 010.
- c]** Explain with circuit, how T-flip-flop can be used in reducing the clock frequency.

Ques 2 A] Attempt any TWO of the following – [6]

- a]** Explain concept of 1-bit memory cell.
- b]** Draw the block diagram of digital computer and explain its function.
- c]** In a circuit of 5-bit R-2R ladder find: (a) full scale output voltage (b) for input 10101, if 0 = 0V and 1 = 10V.

B] Attempt any ONE of the following – [4]

- a]** Design 4:1 multiplexer using two 2:1 multiplexer circuits and explain its working with diagram and truth table.
- b]** State and prove the De Morgan's both theorems.

Ques 3 : A] Attempt any TWO of the following – [6]

- a]** Explain the working of counter type ADC circuit.
- b]** Explain the working of a hard disk used in computers with diagram.
- c]** Draw the circuit of CMOS inverter and explain its working.

B] Attempt any ONE of the following – [4]

- a]** What is a demultiplexer? Design 1:4 Mux using gates and explain its working.

b] Implement the logic expression: $f(A, B, C, D) = \Sigma_m(0, 1, 4, 5, 8, 6, 3, 11, 14)$ and draw necessary diagram also.

Ques 4: A] Attempt any **TWO** of the following – [6]

- a] Draw the circuit of M/S flip-flop and explain its working.
- b] Explain the working of ring counter with diagram.
- c] What are decoders? Explain the working of BCD to decimal decoder.

B] Attempt any **ONE** of the following – [4]

- a] Draw the circuit of asynchronous counter and explain its working with wave diagrams.
- b] Draw the diagram of BCD to decimal decoder with NOT gate and AND gates and explain its working.

Ques 5 A] Attempt any **TWO** of the following – [6]

- a] Discuss the working of Tri-state inverter circuit with diagram and truth table.
- b] Write a short note on shift register.
- c] Draw the circuit diagram of up-down counter and explain its working.

B] Attempt any **ONE** of the following – [4]

- a] Define: fan out, figure of merit, power dissipation, propagation delay.
- b] What is an Ex-OR gate? Thus, explain working of 4-bit controlled inverter.

OR

Ques 5 A] Attempt any **TWO** of the following – [6]

- a] Explain method of converting fractional binary into decimal equivalent, with example.
- b] What are codes? Explain in brief: ASCII and BCD code.
- c] What is MOD of a counter? Explain with one example.

B] Attempt any **ONE** of the following - [4]

- a] Compare TTL and CMOS logic circuits with any four points.
- b] Draw the logic diagram for following logic expression –

$$Y = \overline{A}BC + A\overline{A}D + C\overline{A}D + BAC$$

The End