
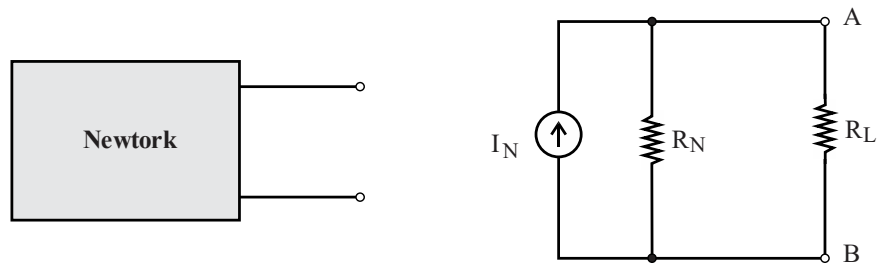


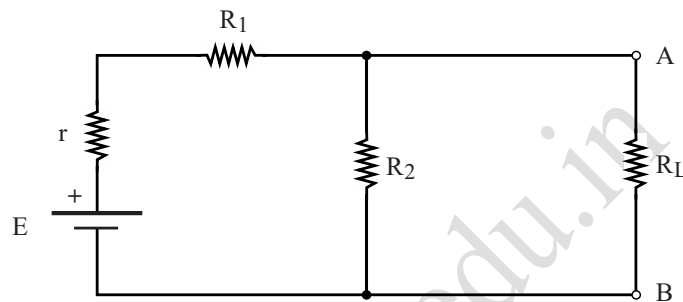1.11.3 Norton's theorem


Statement: A complex network consisting of number of sources of e.m.f. and resistors can be replaced by a single constant current source in parallel with a single resistance or impedance.




Proof Setp-1: Consider the following circuit –



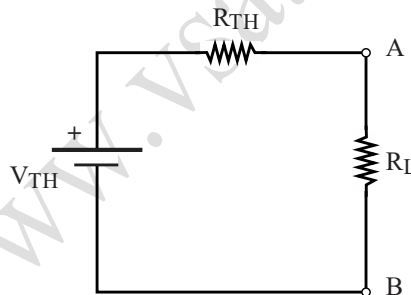We know that the Thevenin's equivalent of this circuit is given as follows:



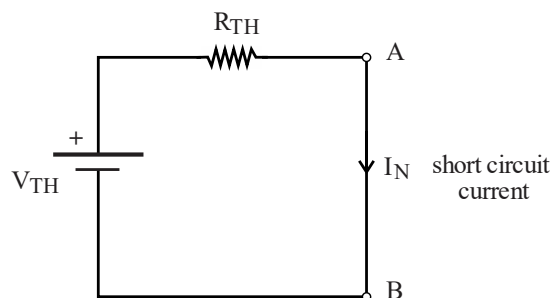
Setp-2: Now remove load resistor from the Thevenin's equivalent circuit and short circuit the terminals A-B, as shown below. So the short circuit current will flow, which is the Norton's current (I_N).



Mathematically we can calculate the Norton's current (I_N) as follows:

$$I_N = \frac{V_{TH}}{R_{TH}}$$

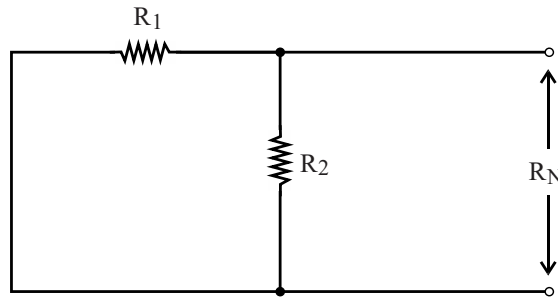Step-3: Now remove the short circuit and the e.m.f. source from the circuit, as follows:




Here the value of R_N is calculated as follows:

$$R_N = R_1 || R_2$$


$$\therefore R_N = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

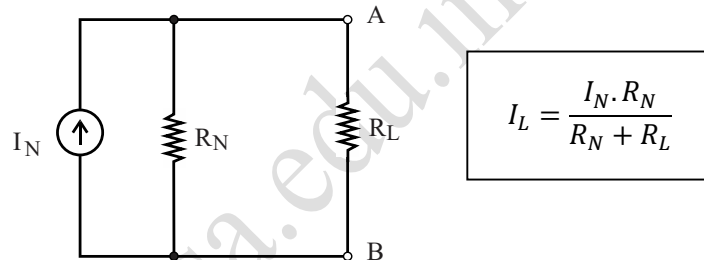Finally the Norton's equivalent circuit is given below. The load current is given by the equation:



EXERCISE

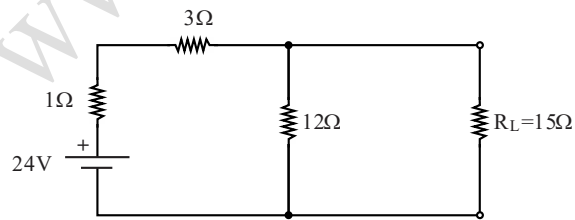- 1) Obtain the Norton's equivalent of following circuit and calculate the current flowing through R_L in following circuit. Use the given equations for the same. Draw Norton's equivalent circuit also. (**Ans: $I_N = 6A$, $R_N = 3\Omega$, $I_L = 1A$**)



- 2) Obtain the Norton's equivalent of following circuit and calculate the current flowing through the load resistor. Draw Norton's equivalent circuit also. (**Ans: $R_N = 6\Omega$, $I_N = 4A$, $I_L = 1.33A$**)

